

Your Name: _____ netid: _____ Group #:
Name: _____ netid: _____
Name: _____ netid: _____
Name: _____ netid: _____

ECE 120 Worksheet 8: Shift registers and Counters

Before you come to discussion, please read Lecture Notes Sections 2.6, 2.7, and 3.1.

In this discussion, you will implement a synchronous counter. You will also design several serial shift registers.

1. Synchronous Counters

- Using D flip-flops, implement a synchronous counter that generates the output sequence

000 \rightarrow 010 \rightarrow 011 \rightarrow 101 \rightarrow 110 \rightarrow 000....

Your answer should consist of a **next-state table**, **K-maps**, **Boolean expressions** (in minimal SOP form) for all D flip-flop inputs, and a **circuit drawing**.

S_2	S_1	S_0	S_2^+	S_1^+	S_0^+
0	0	0	0	1	0
0	0	1	x	x	x
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	x	x	x
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	x	x	x

		S_2S_1			
		00	01	11	10
S_0	0	1	1	0	x
	1	x	0	x	1


		S_2S_1			
		00	01	11	10
S_0	0	0	0	0	x
	1	x	1	x	1

		S_2S_1			
		00	01	11	10
S_0^+	0	0	1	0	x
	1	x	1	x	0

$S_2^+ = S_0$ (a wire)

$S_1^+ = S_1' + S_2' S_0' = (S_1 (S_2' S_0')')'$ (NAND gate implementation)

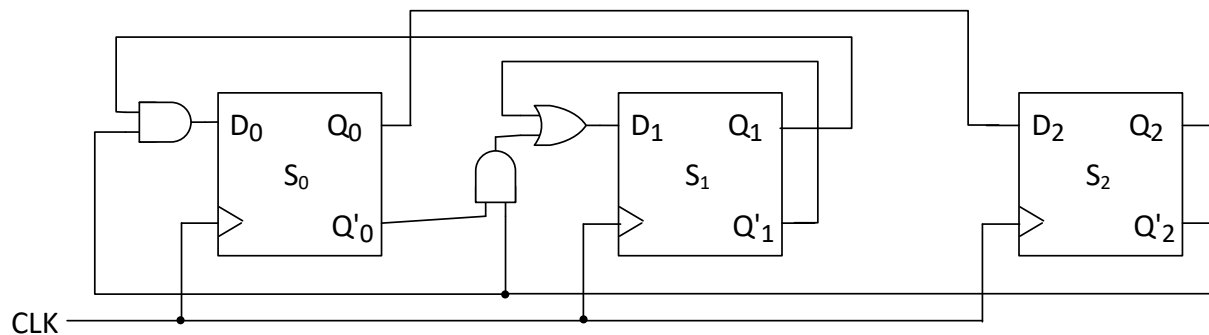$S_0^+ = S_2' S_1 = (S_2 + S_1')'$ (NOR gate implementation)




- A counter is *self-starting* if, regardless of its initial state, the counter eventually enters the desired sequence. Is your counter self-starting? Explain your answer.

For the design above, the unspecified states are 001, 100, and 111. Looking at the equations, we find that 001 \rightarrow 110, 100 \rightarrow 010, and 111 \rightarrow 100, so the counter falls into the desired sequence within two cycles, and the counter is self-starting.


2. Serial shift registers

Draw missing connections to implement various shift registers.

 
1. *Shift right*: All bits of the register move right by one position, and a new bit value from a serial input is stored in the most significant bit (leftmost flip-flop below).



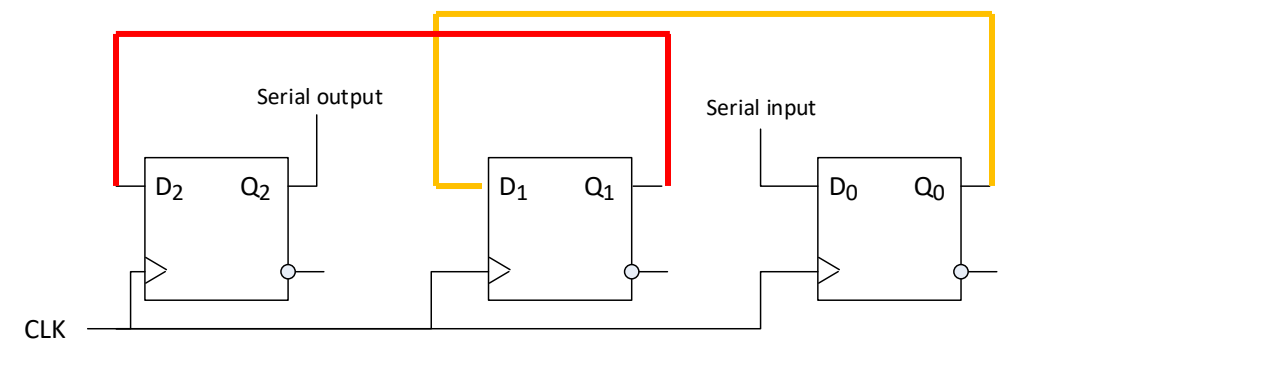
2. *Shift left*: All bits of the register move left by one position, and a new bit value from a serial input is stored in the least significant bit (rightmost flip-flop below).



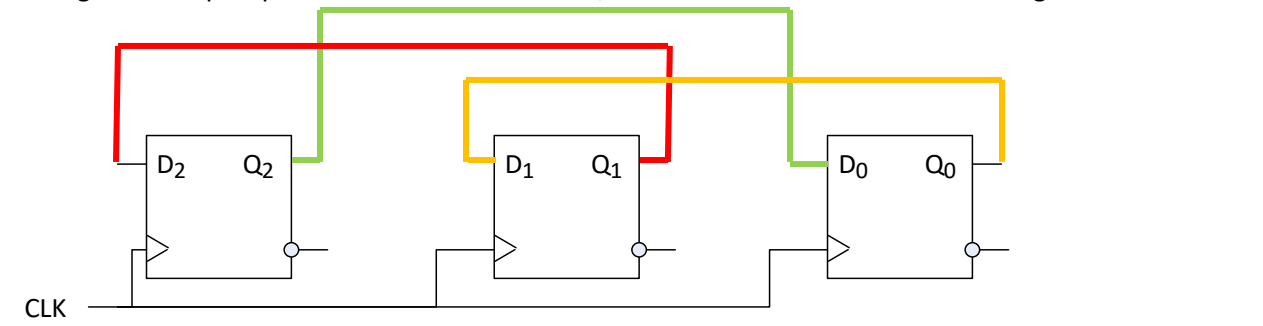
3. *Circular shift left* (also known as rotate left): the output of the leftmost flip-flop feeds back into the rightmost flip-flop. Hence each bit moves left, and the leftmost bit becomes the rightmost bit.



 
4. *Circular shift right* (also known as rotate right): the output of the rightmost flip-flop feeds back into the leftmost flip-flop. Hence each bit moves right, and the rightmost bit becomes the leftmost bit.



 5. *Logical shift right*: The bits in the register are treated as an unsigned number (or simply a set of bits). All bits of the register move right (towards less significant digits) by one position, and a 0 is stored in the most significant bit (leftmost flip-flop below). Logical shift right corresponds to division by 2 for unsigned numbers.



 6. *Arithmetic shift left*: The register contents are treated as a 2's complement number, so a 0 is shifted into the least significant bit (the rightmost flip-flop). Arithmetic shift left corresponds to multiplication by 2 for 2's complement numbers. Notice that *arithmetic* and *logical* shift left are identical.



7. *Arithmetic shift right*: The register contents are treated as a 2's complement number, so the sign bit (leftmost flip-flop below) is copied back into itself. Arithmetic shift right corresponds to division by 2 for 2's complement numbers.

