

Your Name: _____ netid: _____ Group #:
Name: _____ netid: _____
Name: _____ netid: _____
Name: _____ netid: _____

ECE 120 Worksheet 8: Shift registers and Counters

Before you come to discussion, please read Lecture Notes Sections 2.6, 2.7, and 3.1.

In this discussion, you will implement a synchronous counter. You will also design several serial shift registers.

1. Synchronous Counters

- Using D flip-flops, implement a synchronous counter that generates the output sequence

000 \rightarrow 010 \rightarrow 011 \rightarrow 101 \rightarrow 110 \rightarrow 000....

Your answer should consist of a **next-state table**, **K-maps**, **Boolean expressions** (in minimal SOP form) for all D flip-flop inputs, and a **circuit drawing**.

S_2	S_1	S_0	S_2^+	S_1^+	S_0^+
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

		S_2S_1			
		00	01	11	10
S_0	0				
	1				

		S_2S_1			
		00	01	11	10
S_0	0				
	1				

		S_2S_1			
		00	01	11	10
S_0	0				
	1				


$S_2^+ =$ _____ $S_1^+ =$ _____ $S_0^+ =$ _____

- A counter is *self-starting* if, regardless of its initial state, the counter eventually enters the desired sequence. Is your counter self-starting? Explain your answer.


2. Serial shift registers

Draw missing connections to implement various shift registers.

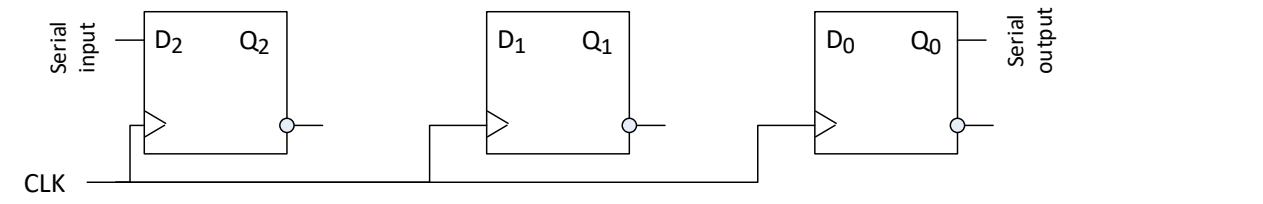
1. *Shift right*: All bits of the register move right by one position, and a new bit value from a serial input is stored in the most significant bit (leftmost flip-flop below).



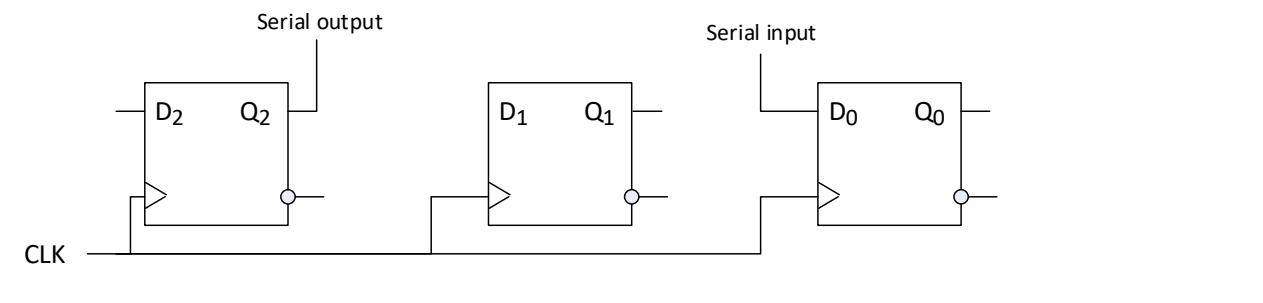
2. *Shift left*: All bits of the register move left by one position, and a new bit value from a serial input is stored in the least significant bit (rightmost flip-flop below).



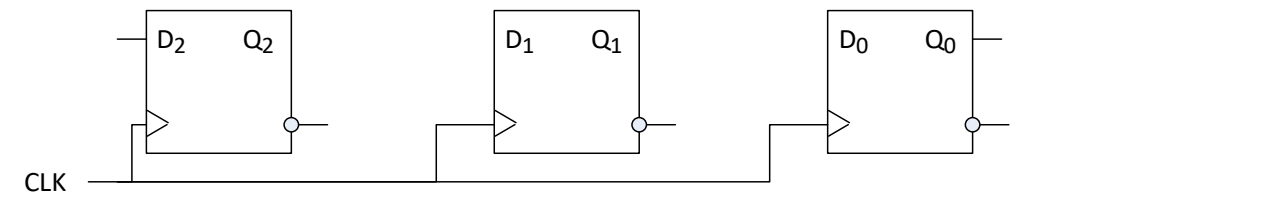
3. *Circular shift left* (also known as rotate left): the output of the leftmost flip-flop feeds back into the rightmost flip-flop. Hence each bit moves left, and the leftmost bit becomes the rightmost bit.



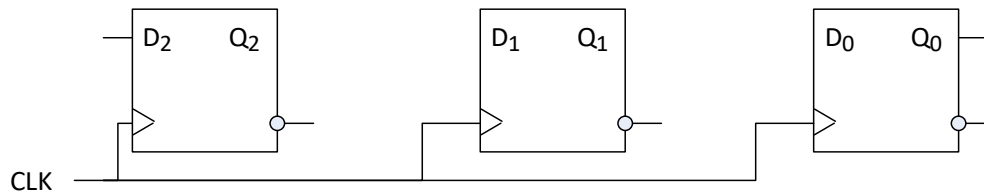
4. *Circular shift right* (also known as rotate right): the output of the rightmost flip-flop feeds back into the leftmost flip-flop. Hence each bit moves right, and the rightmost bit becomes the leftmost bit.



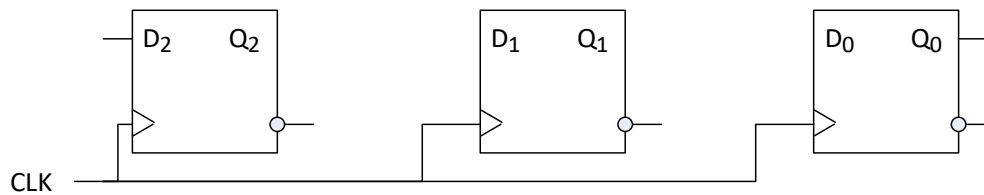5. *Logical shift right*: The bits in the register are treated as an unsigned number (or simply a set of bits). All bits of the register move right (towards less significant digits) by one position, and a 0 is stored in the most significant bit (leftmost flip-flop below). Logical shift right corresponds to division by 2 for unsigned numbers.



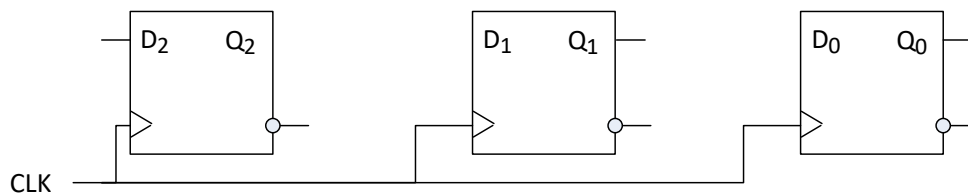6. *Arithmetic shift left*: The register contents are treated as a 2's complement number, so a 0 is shifted into the least significant bit (the rightmost flip-flop). Arithmetic shift left corresponds to multiplication by 2 for 2's complement numbers. Notice that *arithmetic* and *logical* shift left are identical.



7. *Arithmetic shift right*: The register contents are treated as a 2's complement number, so the sign bit (leftmost flip-flop below) is copied back into itself. Arithmetic shift right corresponds to division by 2 for 2's complement numbers.

