

# ECE329 Project #2 Report

Ruiqi Li, 3180111638

January 8, 2021

## 1 Problem 1

**(20 pts) Please derive the analytical solution of  $v(z, t)$  and  $i(z, t)$  assuming  $v_s(t) = V_0 \sin(\omega t)$  so that you do not need to worry about the transient effects. Please show your derivation.**

Since  $\beta l = \beta d = \beta \frac{\lambda}{4} = \beta \frac{2\pi}{4\beta} = \frac{\pi}{2}$ , we have.

$$\Gamma_L = \frac{Z_L - Z_c}{Z_L + Z_c} = \frac{25 - 50}{25 + 50} = -\frac{1}{3} \quad (1)$$

Also, for  $Z_{in}$  we compute it from the formula:

$$Z_{in} = Z(-d) = Z_c \frac{Z_L + jZ_c \tan \beta d}{Z_c + jZ_L \tan \beta d} = \frac{Z_c^2}{Z_L} = 100\Omega \quad (2)$$

Then, using KVL we have:

$$V(-d) = V_s \frac{Z_{in}}{Z_{in} + R_s} = \frac{1}{2} V_s = -j\frac{1}{2} V_0 \quad (3)$$

Substitute this value into  $\tilde{V}(z) = \tilde{V}^+(e^{-j\beta z} + \Gamma_0 e^{j\beta z})$ , we have that  $\tilde{V}^+ = -\frac{3}{8}$ . Similarly we can get the expression for current. Finally:

$$\begin{aligned} \tilde{V}(z) &= -\frac{3}{8} e^{-j\beta z} + \frac{1}{8} e^{j\beta z} \\ \tilde{I}(z) &= -\frac{3}{400} e^{-j\beta z} - \frac{1}{400} e^{j\beta z} \end{aligned}$$

or,

$$\begin{aligned} v(z, t) &= -\frac{3}{8} \cos(\omega t - \beta z) + \frac{1}{8} \cos(\omega t + \beta z) \\ i(z, t) &= -\frac{3}{400} \cos(\omega t - \beta z) - \frac{1}{400} \cos(\omega t + \beta z) \end{aligned}$$

## 2 Problem 2

**Please find the load voltage  $v_L(t) = v(z = 0, t)$ , for  $0 \leq t \leq 10T$  using the FDTD method given  $v_S(t) = V_0 \sin(\omega t) u(t)$ .**

### 2.1 (i)

To normalize the results, assume that  $T = 10\text{s}$  and  $\lambda = 4\text{m}$ . Also, to help simplify the parameters, let  $\Delta z_0 = \frac{1}{20}\lambda$  and  $\Delta t_0 = \frac{\Delta z}{v_p}$ . Here are the results of the simulations:

For  $\Delta z = 2 * \Delta z_0$  and  $\Delta t = 2 * \Delta t_0$ :

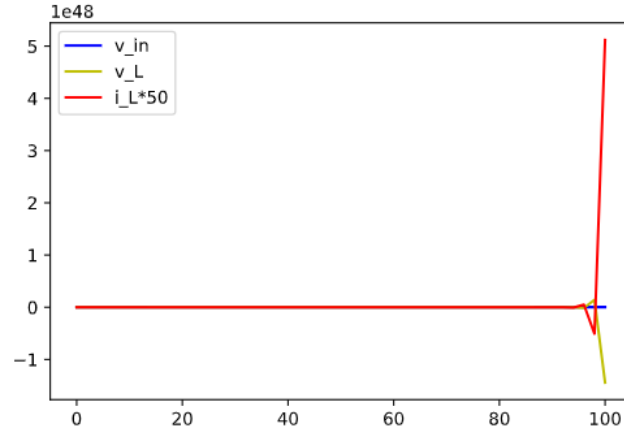


Figure 1: Plot for  $\Delta z = 2 * \Delta z_0$  and  $\Delta t = 2 * \Delta t_0$

For  $\Delta z = \Delta z_0$  and  $\Delta t = \Delta t_0$ :

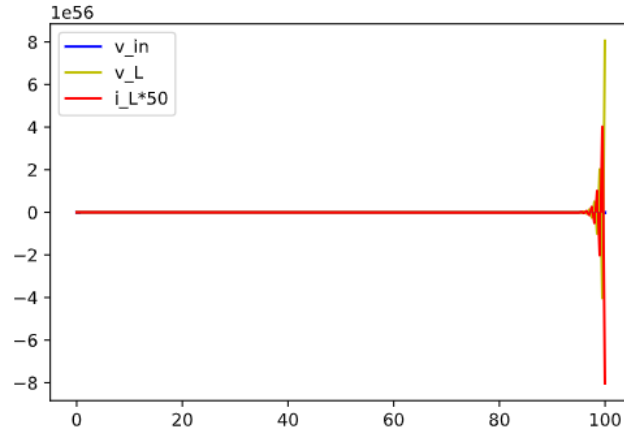


Figure 2: Plot for  $\Delta z = \Delta z_0$  and  $\Delta t = \Delta t_0$

For  $\Delta z = \frac{1}{2} \Delta z_0$  and  $\Delta t = \Delta t_0$ :

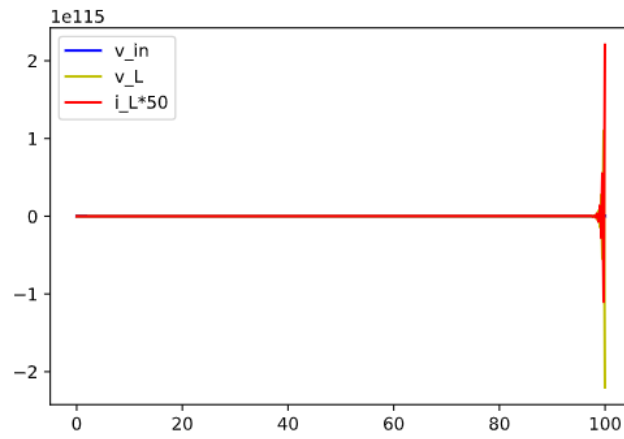


Figure 3: Plot for  $\Delta z = \frac{1}{2} \Delta z_0$  and  $\Delta t = \Delta t_0$

For  $\Delta z = \Delta z_0$  and  $\Delta t = \frac{1}{2} \Delta t_0$ :

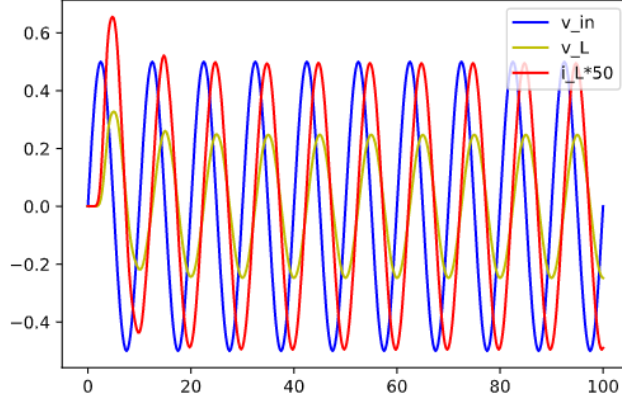


Figure 4: Plot for  $\Delta z = \Delta z_0$  and  $\Delta t = \frac{1}{2}\Delta t_0$

For  $\Delta z = \frac{1}{2}\Delta z_0$  and  $\Delta t = \frac{1}{2}\Delta t_0$ :

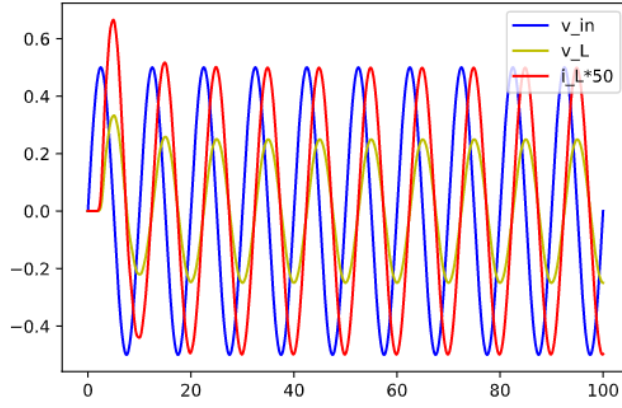


Figure 5: Plot for  $\Delta z = \frac{1}{2}\Delta z_0$  and  $\Delta t = \frac{1}{2}\Delta t_0$

For  $\Delta z = \frac{1}{5}\Delta z_0$  and  $\Delta t = \frac{1}{5}\Delta t_0$ :

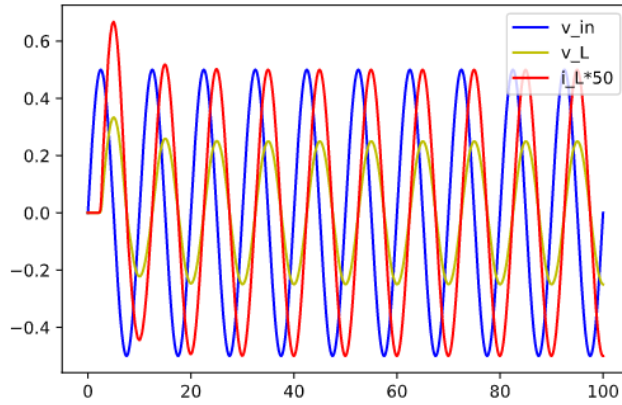


Figure 6: Plot for  $\Delta z = \frac{1}{5}\Delta z_0$  and  $\Delta t = \frac{1}{5}\Delta t_0$

From above we can see that as  $\Delta z$  and  $\Delta t$  decrease, the accuracy and stability both increase. Also, it seems that  $\Delta t$  is more significant than  $\Delta z$  when concerning stability. Considering accuracy, stability and efficiency, we choose  $\Delta z = \frac{1}{2}\Delta z_0$  and  $\Delta t = \frac{1}{2}\Delta t_0$ . The comparison between the numerical results and the analytical results are shown below:

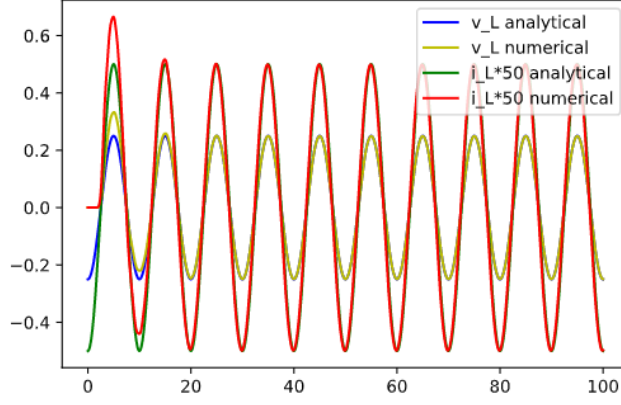


Figure 7: Comparison between Numerical and Analytical Results using  $\Delta z = \frac{1}{2}\Delta z_0$  and  $\Delta t = \frac{1}{2}\Delta t_0$

It's obvious that they converge well after only about 1.5 cycles.

## 2.2 (ii)

The comparison result is shown as Figure 7. The numerical solution converges well.

## 2.3 (iii)

If  $d = 0$ , then  $V_L(t) = V_s \frac{R_L}{R_L + R_s} = \frac{1}{5} \sin(\omega t)u(t)$ , and  $I_L(t) = \frac{V_L}{R_L} = \frac{1}{125} \sin(\omega t)u(t)$ .

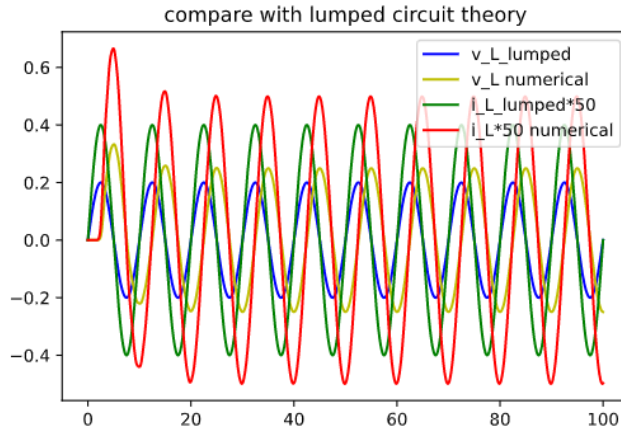


Figure 8: Comparison between the Results with the Lumped Circuit Theory Results using  $\Delta z = \frac{1}{2}\Delta z_0$  and  $\Delta t = \frac{1}{2}\Delta t_0$

It shows that not only the amplitude is decreases from the lumped circuit theory results to the numerical results, the phase is also shifted.

## 3 Problem 3

All the results are shown below:

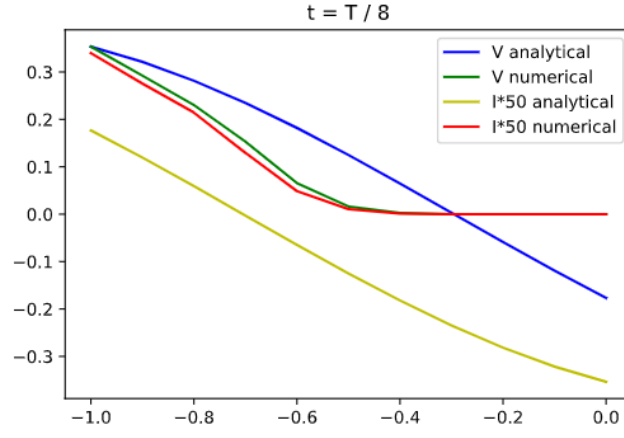


Figure 9: Comparison between Numerical and Analytical with  $t = \frac{T}{8}$

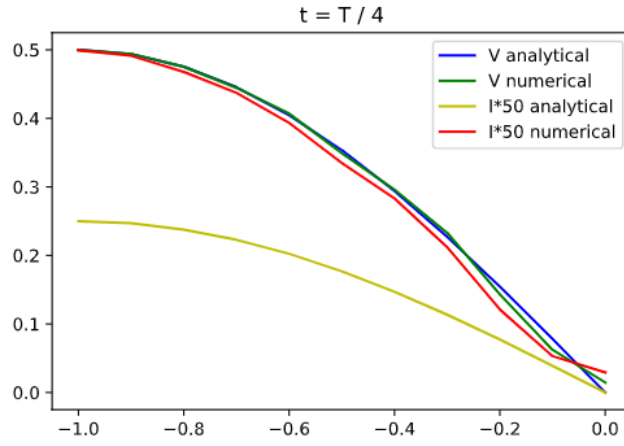


Figure 10: Comparison between Numerical and Analytical with  $t = \frac{T}{4}$

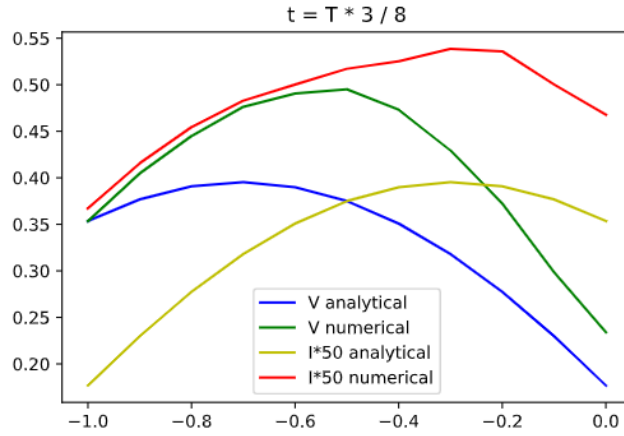


Figure 11: Comparison between Numerical and Analytical with  $t = \frac{3T}{8}$

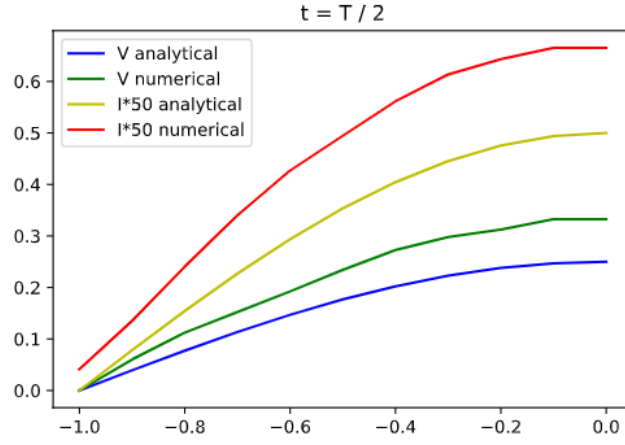


Figure 12: Comparison between Numerical and Analytical with  $t = \frac{T}{2}$

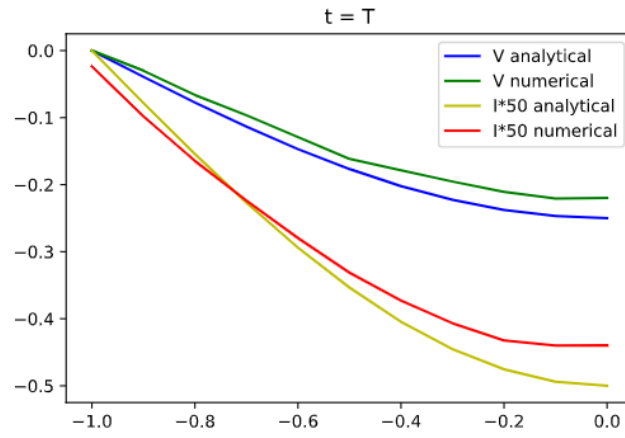


Figure 13: Comparison between Numerical and Analytical with  $t = T$

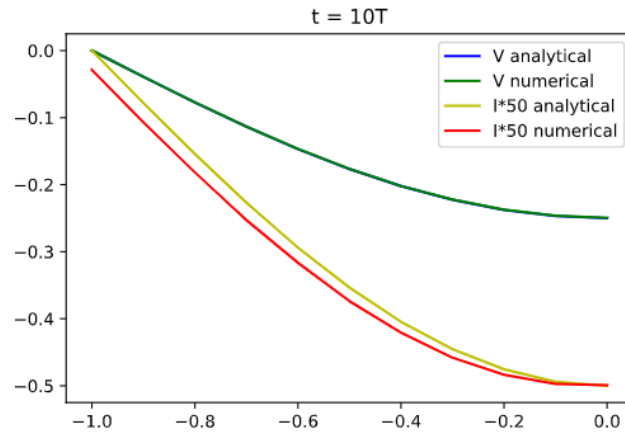


Figure 14: Comparison between Numerical and Analytical with  $t = 10T$

As shown above, it takes some time for the simulation to be stable. About 1 period is enough.