

Your Name: \_\_\_\_\_ netid: \_\_\_\_\_  
 Name: \_\_\_\_\_ netid: \_\_\_\_\_  
 Name: \_\_\_\_\_ netid: \_\_\_\_\_  
 Name: \_\_\_\_\_ netid: \_\_\_\_\_

Group #:

## ECE 120 Worksheet 5: From Problem Statement to Digital Circuit

Before you begin today's discussion, be sure that you are familiar with terminology, such as literals, minterms, maxterms, canonical forms, implicants, prime implicants, and K-maps. Also be sure that you know how to find canonical SOP and POS forms for Boolean functions, and that you know how to use K-maps. To check these skills, you can make up a truth table at random, find a Boolean expression for the function, then check your result by writing a truth table for your expression.

**Use the area heuristic**—number of literals plus the number of operators, not including complemented literals—to find minimal expressions in today's problems. Choosing a minimal number of prime implicants from a K-map will give you minimal solutions in this sense.

**Truth table for Problem 1**

| <i>A</i> | <i>B</i> | <i>C</i> | <i>D</i> | <i>V</i> |
|----------|----------|----------|----------|----------|
| 0        | 0        | 0        | 0        |          |
| 0        | 0        | 0        | 1        |          |
| 0        | 0        | 1        | 0        |          |
| 0        | 0        | 1        | 1        |          |
| 0        | 1        | 0        | 0        |          |
| 0        | 1        | 0        | 1        |          |
| 0        | 1        | 1        | 0        |          |
| 0        | 1        | 1        | 1        |          |
| 1        | 0        | 0        | 0        |          |
| 1        | 0        | 0        | 1        |          |
| 1        | 0        | 1        | 0        |          |
| 1        | 0        | 1        | 1        |          |
| 1        | 1        | 0        | 0        |          |
| 1        | 1        | 0        | 1        |          |
| 1        | 1        | 1        | 0        |          |
| 1        | 1        | 1        | 1        |          |

**K-map for Problem 1**

|           |    |           |    |    |    |
|-----------|----|-----------|----|----|----|
|           |    | <i>AB</i> |    |    |    |
|           |    | 00        | 01 | 11 | 10 |
| <i>CD</i> | 00 |           |    |    |    |
|           | 01 |           |    |    |    |
|           | 11 |           |    |    |    |
|           | 10 |           |    |    |    |

## 1. From Problem Statement to Digital Circuit

You may have noticed that the carry out of a one-bit adder is a majority function of the two addends and the carry in. In other words, the carry out is a 1 whenever two or more of the inputs are 1s.

Let's design a majority voting unit to calculate the outcome of a vote by a committee of four members,  $A$ ,  $B$ ,  $C$ , and  $D$ . For each member, a value of 1 means a yes vote, and a value of 0 means a no vote. Let's use the same convention for the vote result  $V(A,B,C,D)$ .

Sadly, a committee size of four can result in a tied vote, so let's say that, in such cases, the vote  $V$  goes with  $A$ 's vote.

- a. Can you write down  $V$  as a function of  $A$ ,  $B$ ,  $C$ , and  $D$  by just thinking the problem through? It's ok if your answer is, "No," but think about the question.
- b. Fill in the truth table on the previous page, then look at the truth table to answer these questions:
  - i. How many product terms appear in the canonical SOP form of  $V$ ?  
(Note: you do **not** need to write down the canonical SOP form.)
  - ii. How many sum terms appear in the canonical POS form of  $V$ ?  
(Note: Again, you do **not** need to write down the canonical POS form.)
- c. Copy the bits from the truth table to the K-map. Be careful with ordering. Then use the K-map to find a minimal SOP expression for  $V$ .
- d. Draw the circuit using AND and OR gates. (You should only need five gates.)


## 2. A Simple Thermal Controller

Prof. Lumetta needs some help with the water heater in his home. The design is as follows. The unit has a control dial that allows the user to set the desired temperature using a two-bit unsigned value  $C_1C_0$ . A temperature sensor reads the current water temperature, also as a two-bit unsigned value  $T_1T_0$ . A digital circuit, which you must design, then decides whether to turn on a heating element or not. The heating element is controlled by logic signal  $H$ , which should be set as follows:

$$H = \begin{cases} 0 & \text{if } T \geq C \\ 1 & \text{if } T < C \end{cases}$$

a. Fill in the truth table below for function  $H$ .

| $C_1$ | $C_0$ | $T_1$ | $T_0$ | $H$ |
|-------|-------|-------|-------|-----|
| 0     | 0     | 0     | 0     |     |
| 0     | 0     | 0     | 1     |     |
| 0     | 0     | 1     | 0     |     |
| 0     | 0     | 1     | 1     |     |
| 0     | 1     | 0     | 0     |     |
| 0     | 1     | 0     | 1     |     |
| 0     | 1     | 1     | 0     |     |
| 0     | 1     | 1     | 1     |     |
| 1     | 0     | 0     | 0     |     |
| 1     | 0     | 0     | 1     |     |
| 1     | 0     | 1     | 0     |     |
| 1     | 0     | 1     | 1     |     |
| 1     | 1     | 0     | 0     |     |
| 1     | 1     | 0     | 1     |     |
| 1     | 1     | 1     | 0     |     |
| 1     | 1     | 1     | 1     |     |

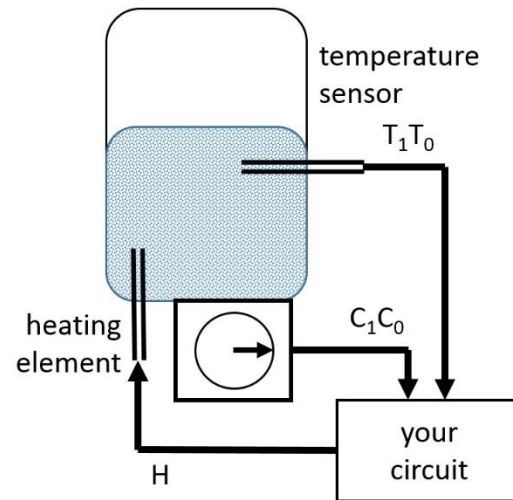

|          |    | $C_1C_0$ |    |    |    |
|----------|----|----------|----|----|----|
|          |    | 00       | 01 | 11 | 10 |
| $T_1T_0$ | 00 |          |    |    |    |
|          | 01 |          |    |    |    |
|          | 11 |          |    |    |    |
|          | 10 |          |    |    |    |

- Copy the bits from the truth table to the K-map above. Be careful with ordering.
- Use the K-map to find a minimal SOP expression for  $H$ .

### 3. Two-bit Thermal Control

Prof. Lumetta has issues. Apparently, the thermal control circuit that you designed for Part 2 today doesn't quite solve the problem. His water heater radiates too much heat. So we need to use a two-bit unsigned output  $H_1H_0$  and keep the heat on at a low level even when the temperature reaches the desired level.

Remember that the inputs provided by the system are a control dial that allows the user to set the desired temperature using a two-bit unsigned value  $C_1C_0$ , and a temperature sensor that reads the current water temperature, also as a two-bit unsigned value  $T_1T_0$ .

Your function  $H$  should then be given by:

$$H = \begin{cases} \min(3, C - T + 1) & \text{if } T \leq C \\ 0 & \text{if } T > C \end{cases}$$

The use of the minimum function ensures that we do not try to set the heat to 4 when  $C$  is 3 and  $T$  is 0.

Fill in the K-maps below, then derive minimal expressions for  $H_1$  and  $H_0$ . *Hints:  $H_1$  should be quite easy. For  $H_0$ , consider both SOP and POS expressions, and use the better of the two.*

**$H_1$**

|          |    | $C_1C_0$ |    |    |    |
|----------|----|----------|----|----|----|
|          |    | 00       | 01 | 11 | 10 |
| $T_1T_0$ | 00 |          |    |    |    |
|          | 01 |          |    |    |    |
|          | 11 |          |    |    |    |
|          | 10 |          |    |    |    |

**$H_0$**

|          |    | $C_1C_0$ |    |    |    |
|----------|----|----------|----|----|----|
|          |    | 00       | 01 | 11 | 10 |
| $T_1T_0$ | 00 |          |    |    |    |
|          | 01 |          |    |    |    |
|          | 11 |          |    |    |    |
|          | 10 |          |    |    |    |