

**ECE 120 Second Midterm Exam
Fall 2016**

Tuesday, October 18, 2016

Name: _____

NetID: _____

Discussion Section:

9:00 AM		
10:00 AM		
11:00 AM	<input type="checkbox"/> AB1	<input type="checkbox"/> AB8
12:00 PM	<input type="checkbox"/> AB2	<input type="checkbox"/> AB9
1:00 PM	<input type="checkbox"/> AB3	<input type="checkbox"/> ABA
2:00 PM	<input type="checkbox"/> AB4	<input type="checkbox"/> ABB
3:00 PM	<input type="checkbox"/> AB5	
4:00 PM	<input type="checkbox"/> AB6	<input type="checkbox"/> ABC
5:00 PM	<input type="checkbox"/> AB7	<input type="checkbox"/> ABD

- Be sure that your exam booklet has 11 pages.
- Write your name, netid and check discussion section on the title page.
- Do not tear the exam booklet apart, except for the last two pages.
- Use backs of pages for scratch work if needed.
- This is a closed book exam. You may not use a calculator.
- You are allowed one handwritten 8.5 x 11" sheet of notes (both sides).
- Absolutely no interaction between students is allowed.
- Clearly indicate any assumptions that you make.
- The questions are not weighted equally. Budget your time accordingly.
- Show your work.

Problem 1 14 points _____

Problem 2 14 points _____

Problem 3 14 points _____

Problem 4 14 points _____

Problem 5 14 points _____

Problem 6 30 points _____

Total 100 points _____

Problem 1 (14 points): K-maps and Don't Cares

Consider the 4-variable function $f(a,b,c,d)$, with the following K-map (drawn twice). **Note:** there are extra copies of this K-map on the last page of the exam. Use them for scratch work, but they will NOT be graded. Make sure you mark the two K-maps below correctly.

Minimal SOP

$f(a,b,c,d)$		cd			
		00	01	11	10
ab	00	1	0	0	1
	01	X	0	0	0
	11	0	X	X	0
	10	X	1	1	X

Minimal POS

$f(a,b,c,d)$		cd			
		00	01	11	10
ab	00	1	0	0	1
	01	X	0	0	0
	11	0	X	X	0
	10	X	1	1	X

1. (4 points) Give a **minimal SOP** expression for $f(a,b,c,d)$ and show the corresponding loops on the **left map**.

Minimal SOP: $f(a,b,c,d) = \underline{\hspace{10cm}}$

2. (3 points) Is the solution to part 1 unique? If it is not, write a different minimal SOP solution.

Circle one: **UNIQUE** **NOT UNIQUE**

If not unique, write a different minimal SOP solution (but do not mark the loops):

Minimal SOP: $f(a,b,c,d) = \underline{\hspace{10cm}}$

3. (4 points) Give a **minimal POS** expression for $f(a,b,c,d)$ and show the corresponding loops on the **right map**.

Minimal POS: $f(a,b,c,d) = \underline{\hspace{10cm}}$

4. (3 points) Is the solution to part 3 unique? If it is not, write a different minimal POS solution.


Circle one: **UNIQUE** **NOT UNIQUE**

If not unique, write a different minimal POS solution (but do not mark the loops):

Minimal POS: $f(a,b,c,d) = \underline{\hspace{10cm}}$

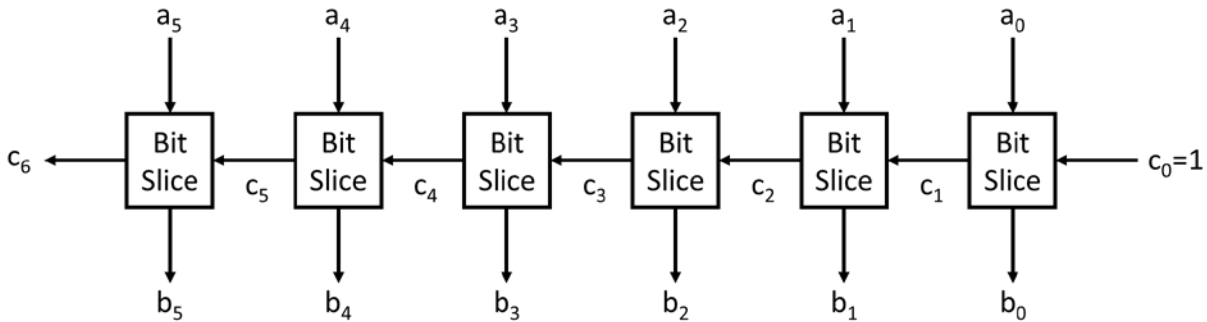Problem 2 (14 points): Bit-sliced Design

The circuit shown below is intended to negate a 6-bit 2's complement number. For example, if the input $a_5a_4a_3a_2a_1a_0 = 110100$, then the output $b_5b_4b_3b_2b_1b_0 = 001100$. Note that the initial carry-in bit c_0 is set to 1 in this design.



1. **(8 points)** Each bit slice is identical. Complete the truth table for a single bit slice and write the minimal SOP expressions.

c_i	a_i	c_{i+1}	b_i
0	0		
0	1		
1	0		
1	1		

Minimal SOP: $c_{i+1} =$ _____

Minimal SOP: $b_i =$ _____


2. **(6 points)** Assume that the b_i and c_{i+1} outputs of each bit slice are implemented using 2-level AND-OR networks based on their minimal SOP expressions. **In this question, count AND and OR gates, but do not count NOT gates.**

How many gates are required in the entire circuit (all bit slices)? _____

How many gates are there along one of the longest paths from a_0 to b_5 ? _____

Problem 3 (14 points): Sequential Feedback Analysis

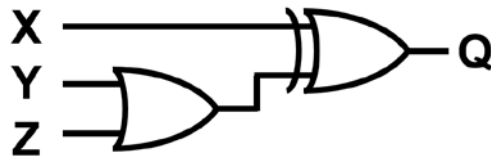
1. **(8 points)** Complete the truth table for the circuit shown below made out of one OR gate and one XOR gate.



X	Y	Z	Q
0	0	0	
0	0	1	
0	1	0	
0	1	1	

X	Y	Z	Q
1	0	0	
1	0	1	
1	1	0	
1	1	1	

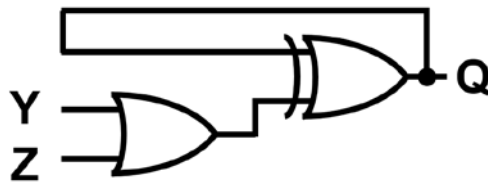2. **(6 points)** For the circuit shown below, which combinations of inputs YZ cause the output Q to oscillate between 0 and 1? In other words, which values of YZ prevent the output Q from holding a stable value?



Circle all oscillating input combinations YZ:

00

01

10


11

Problem 4 (14 points): CMOS Gates, Boolean Expressions and 2-Level Design

1. (6 points) The transistor-level circuit below implements the logic equation:

$$X = \overline{AB} + C$$

Label the inputs to all transistors.

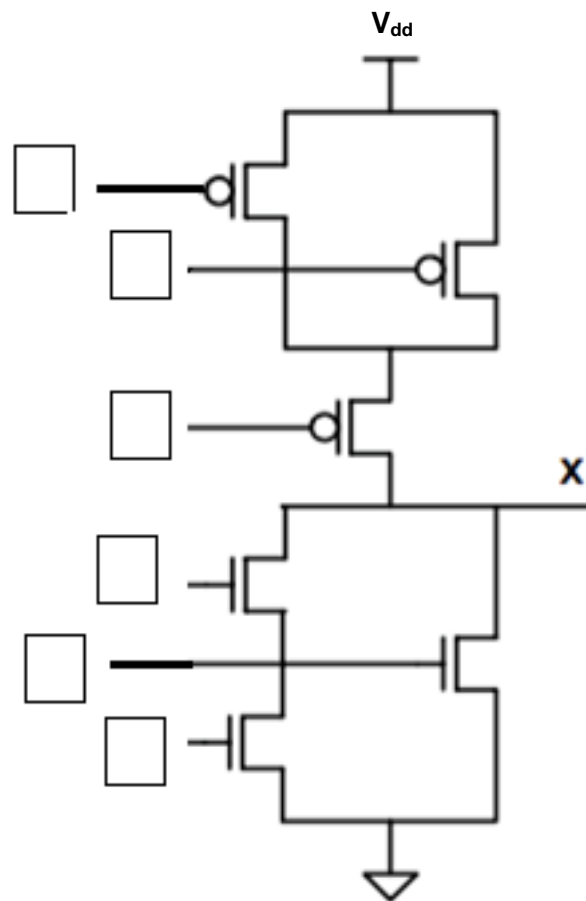

Problem 4 (14 points), continued:

2. **(4 points)** As a consultant to the company Dontel Corp., your task is to design a system that counts the number of 1s present in a 3-bit pattern ABC to output a two-bit number $X_1 X_0$ (representing that count in binary). Describe the behavior of your system as a truth table.

A	B	C	X_1	X_0
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		


3. **(4 points)** Implement $f=wx+y'+xz$ as a 2-level NAND-NAND circuit using the minimum number of gates.

Problem 5 (14 points): Basic Registers

Consider a 3-bit shift register that has the functionality specified in the table to the right.

1. **(10 points)** Label the inputs to the muxes to complete the design of this 3-bit register that performs the operations listed in the table. Parallel load input i is labeled as P_i . **Use labels and do not draw any additional gates or wires.**

F_1	F_0	Operation
0	0	Arithmetic right shift
0	1	Circular shift left
1	0	Arithmetic shift left
1	1	Parallel load

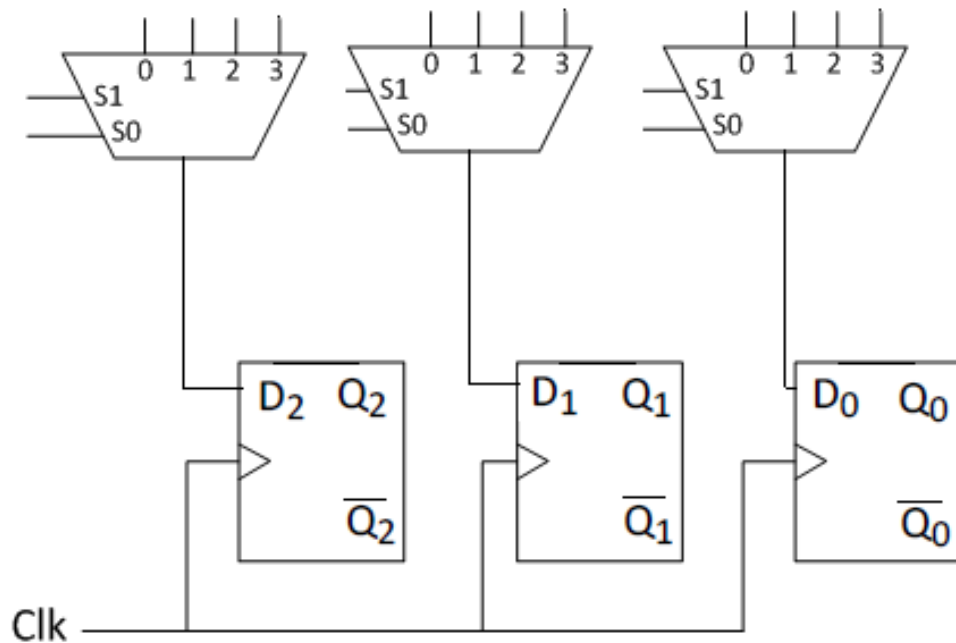

2. **(2 points)** If the shift register initially stores 110, what is stored in the register after one clock cycle when $F_1F_0 = 00$?

Answer: _____

3. **(2 points)** Assume again that 110 is stored in the register. What is stored in the register after one clock cycle when $F_1F_0 = 10$?


Answer: _____

Problem 6 (30 points): Designing Logic with Components


Prof. Lumetta needs your help again. He is still fixated on calculating grades.

Parts 1 through 4 do not depend on one another.

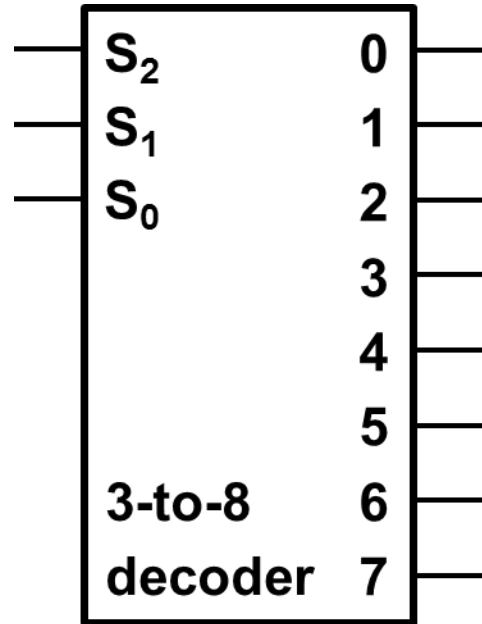1. **(8 points)** Help Prof. Lumetta use a decoder to translate the letter grade (A, B, C, D, or F) into a baseline GPA value. The typed ASCII letter is given as 7-bit input $G = G_6G_5G_4G_3G_2G_1G_0$. The letter 'A' has ASCII code 0x41, 'B' is 0x42, and so forth. **Label decoder inputs and outputs as necessary on the 3-to-8 decoder to the right** to produce signals for the grades A, B, C, D, and F based on bits of input G. Leave any unused decoder outputs unlabeled.



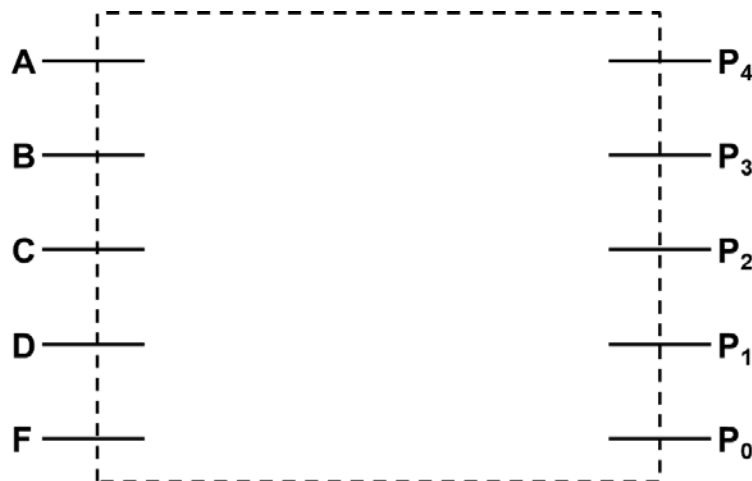2. **(8 points)** Now use the grade signals A, B, C, D, and F to compute a 5-bit 2's complement GPA value P. The grade A has decimal value 12, B has value 9, C has value 6, D has value 3, and F has value 0. You may use **up to five gates** of any type (AND, OR, NOT, XOR, NAND, NOR, or XNOR) as well as **logic values 0 and 1**.



Problem 6 (30 points), continued:

3. (6 points) Grades can be modified by a + or a -. For example, B+ or A-. Process a second 7-bit ASCII character $Q=Q_6Q_5Q_4Q_3Q_2Q_1Q_0$, which is always one of the following: '+' (ASCII code 0x2B), '-' (0x2D), or SPACE (0x20). Design a circuit to produce a 5-bit 2's complement GPA modifier M. M should have a decimal value of 1 when Q is '+', a value of -1 when Q is '-', and a value of 0 when Q is SPACE. Design your circuit to the right using only labels (no components, and no gates). In other words, **label each output bit with an appropriate input variable**.

_____ M_4 _____ M_3 _____ M_2 _____ M_1 _____ M_0

4. (8 points) Prof. Lumetta stores a sum of GPA values in a 5-bit register, R. Using the values that you have computed, P and M, and the current sum R, you must now design a circuit to produce a new sum, T. **Use only combinational logic components** that you have seen in class, such as adders, comparators, muxes, and decoders. Draw your circuit in the box below, **labeling all inputs, outputs, and components clearly, including the number of bits in each signal**. Do not worry about overflow for this problem.

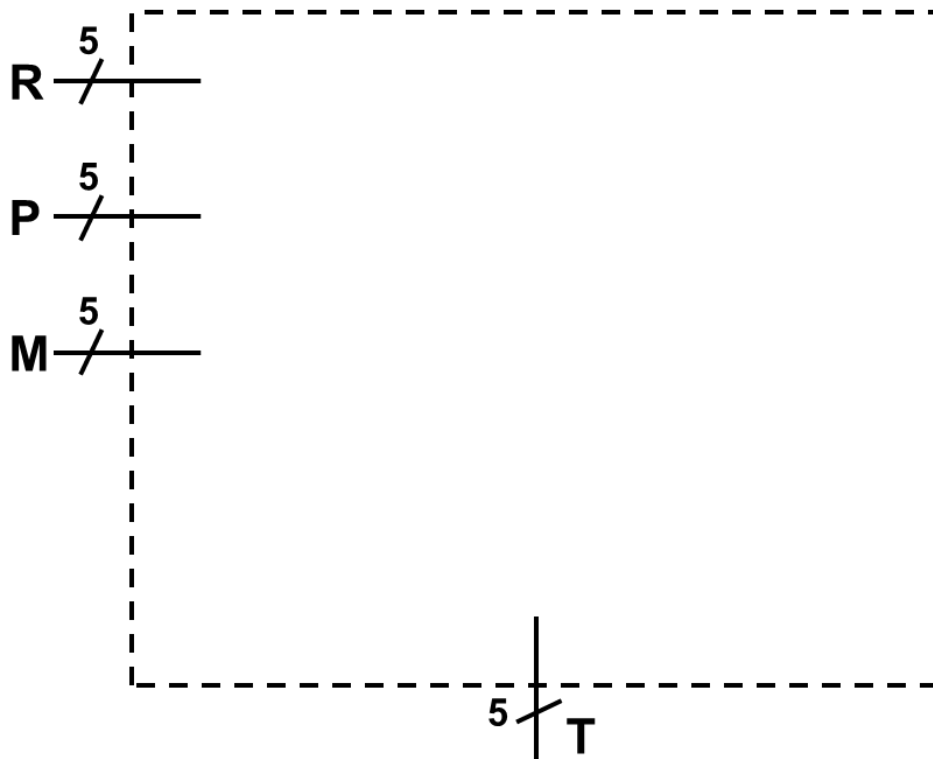


Table of ASCII Characters

Char	Dec	Hex	Char	Dec	Hex	Char	Dec	Hex	Char	Dec	Hex
(nul)	0	00	(sp)	32	20	@	64	40	`	96	60
(soh)	1	01	!	33	21	A	65	41	a	97	61
(stx)	2	02	"	34	22	B	66	42	b	98	62
(etx)	3	03	#	35	23	C	67	43	c	99	63
(eot)	4	04	\$	36	24	D	68	44	d	100	64
(enq)	5	05	%	37	25	E	69	45	e	101	65
(ack)	6	06	&	38	26	F	70	46	f	102	66
(bel)	7	07	'	39	27	G	71	47	g	103	67
(bs)	8	08	(40	28	H	72	48	h	104	68
(ht)	9	09)	41	29	I	73	49	i	105	69
(lf)	10	0a	*	42	2a	J	74	4a	j	106	6a
(vt)	11	0b	+	43	2b	K	75	4b	k	107	6b
(ff)	12	0c	,	44	2c	L	76	4c	l	108	6c
(cr)	13	0d	-	45	2d	M	77	4d	m	109	6d
(so)	14	0e	.	46	2e	N	78	4e	n	110	6e
(si)	15	0f	/	47	2f	O	79	4f	o	111	6f
(dle)	16	10	0	48	30	P	80	50	p	112	70
(dc1)	17	11	1	49	31	Q	81	51	q	113	71
(dc2)	18	12	2	50	32	R	82	52	r	114	72
(dc3)	19	13	3	51	33	S	83	53	s	115	73
(dc4)	20	14	4	52	34	T	84	54	t	116	74
(nak)	21	15	5	53	35	U	85	55	u	117	75
(syn)	22	16	6	54	36	V	86	56	v	118	76
(etb)	23	17	7	55	37	W	87	57	w	119	77
(can)	24	18	8	56	38	X	88	58	x	120	78
(em)	25	19	9	57	39	Y	89	59	y	121	79
(sub)	26	1a	:	58	3a	Z	90	5a	z	122	7a
(esc)	27	1b	;	59	3b	[91	5b	{	123	7b
(fs)	28	1c	<	60	3c	\	92	5c		124	7c
(gs)	29	1d	=	61	3d]	93	5d	}	125	7d
(rs)	30	1e	>	62	3e	^	94	5e	~	126	7e
(us)	31	1f	?	63	3f	_	95	5f	(del)	127	7f

Boolean algebra properties

Commutativity	$x \cdot y = y \cdot x$	$x + y = y + x$
Associativity	$(x \cdot y) \cdot z = x \cdot (y \cdot z)$	$(x + y) + z = x + (y + z)$
Distributivity	$x \cdot (y + z) = x \cdot y + x \cdot z$	$x + y \cdot z = (x + y) \cdot (x + z)$
Idempotence	$x \cdot x = x$	$x + x = x$
Identity	$x \cdot 1 = x$	$x + 0 = x$
Null	$x \cdot 0 = 0$	$x + 1 = 1$
Complementarity	$x \cdot x' = 0$	$x + x' = 1$
Involution		$(x')' = x$
DeMorgan's	$(x \cdot y)' = x' + y'$	$(x + y)' = x' \cdot y'$
Absorption	$x \cdot (x + y) = x$	$x + x \cdot y = x$
No-Name	$x \cdot (x' + y) = x \cdot y$	$x + x' \cdot y = x + y$
Consensus	$(x + y) \cdot (y + z) \cdot (x' + z) = (x + y) \cdot (x' + z)$	$x \cdot y + y \cdot z + x' \cdot z = x \cdot y + x' \cdot z$

Feel free to tear this page off and use it as scratch paper.

Extra copies of K-map for problem 1 (use as scratch copies, we will NOT grade them)

Minimal SOP

$f(a,b,c,d)$		cd			
		00	01	11	10
ab	00	1	0	0	1
	01	X	0	0	0
	11	0	X	X	0
	10	X	1	1	X

Minimal POS

$f(a,b,c,d)$		cd			
		00	01	11	10
ab	00	1	0	0	1
	01	X	0	0	0
	11	0	X	X	0
	10	X	1	1	X

Minimal SOP

$f(a,b,c,d)$		cd			
		00	01	11	10
ab	00	1	0	0	1
	01	X	0	0	0
	11	0	X	X	0
	10	X	1	1	X

Minimal POS

$f(a,b,c,d)$		cd			
		00	01	11	10
ab	00	1	0	0	1
	01	X	0	0	0
	11	0	X	X	0
	10	X	1	1	X

Minimal SOP

$f(a,b,c,d)$		cd			
		00	01	11	10
ab	00	1	0	0	1
	01	X	0	0	0
	11	0	X	X	0
	10	X	1	1	X

Minimal POS

$f(a,b,c,d)$		cd			
		00	01	11	10
ab	00	1	0	0	1
	01	X	0	0	0
	11	0	X	X	0
	10	X	1	1	X